



**KTH Informations- och
kommunikationsteknik**

IE1204 Digital Design


L8: Memory Elements: Latches and Flip-Flops. Counter

Elena Dubrova
KTH / ICT / ES
dubrova@kth.se

This lecture

- BV pp. 383-418, 469-471

Sequential System

 

A sequential system has a built-in memory - the output depends therefore BOTH on the current and previous value(s) of the input signal


Lecture 8 - Lecture 13

How do we get the hardware to remember something?

- To remember something, we have to somehow retain the information
- One way is to store information in the form of a charge on a capacitance (DRAM)
- Another way is to let the information "run around in a circle and bit its own tail"

SR-latch (NOR)

 - SR-latch can be implemented with NOR gates
- SET and RESET inputs are active high
- SET and RESET should not be active at the same time!




(A) Circuit

S	R	Q _a	Q _b	
0	0	0/1	1/0	(No change)
0	1	0	1	
1	0	1	0	
1	1	0	0	Prohibited input combination (causes oscillation)

 (B) Characteristic Table

SR-latch (NAND)


- SR-latch can also be implemented with NAND gates
- SET and RESET inputs are active low




S	R	Q_a	Q_b	
0	0	1	1	Prohibited input combination
0	1	1	0	
1	0	0	1	
1	1	0/1	1/0	(No change)

Construction of clocked latch

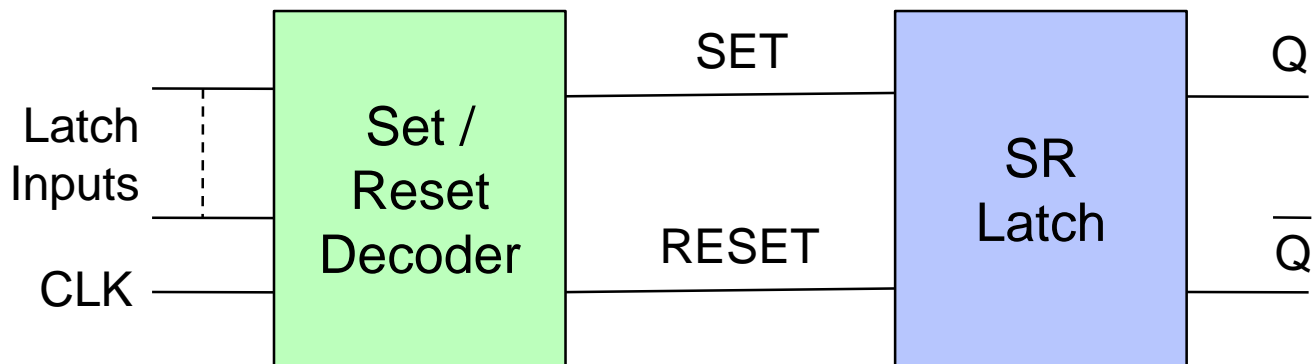- To ensure that the state can only be changed at certain points in time, a special *Clock* signal is used




Gated SR-Latch

 

Clk	S	R	Q(t+1)
0	x	x	Q(t) (no change)
1	0	0	Q(t) (no change)
1	0	1	0
1	1	0	1
1	1	1	x

"Prohibited location"


Gated D-Latch

 

Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

Setup & Hold Time

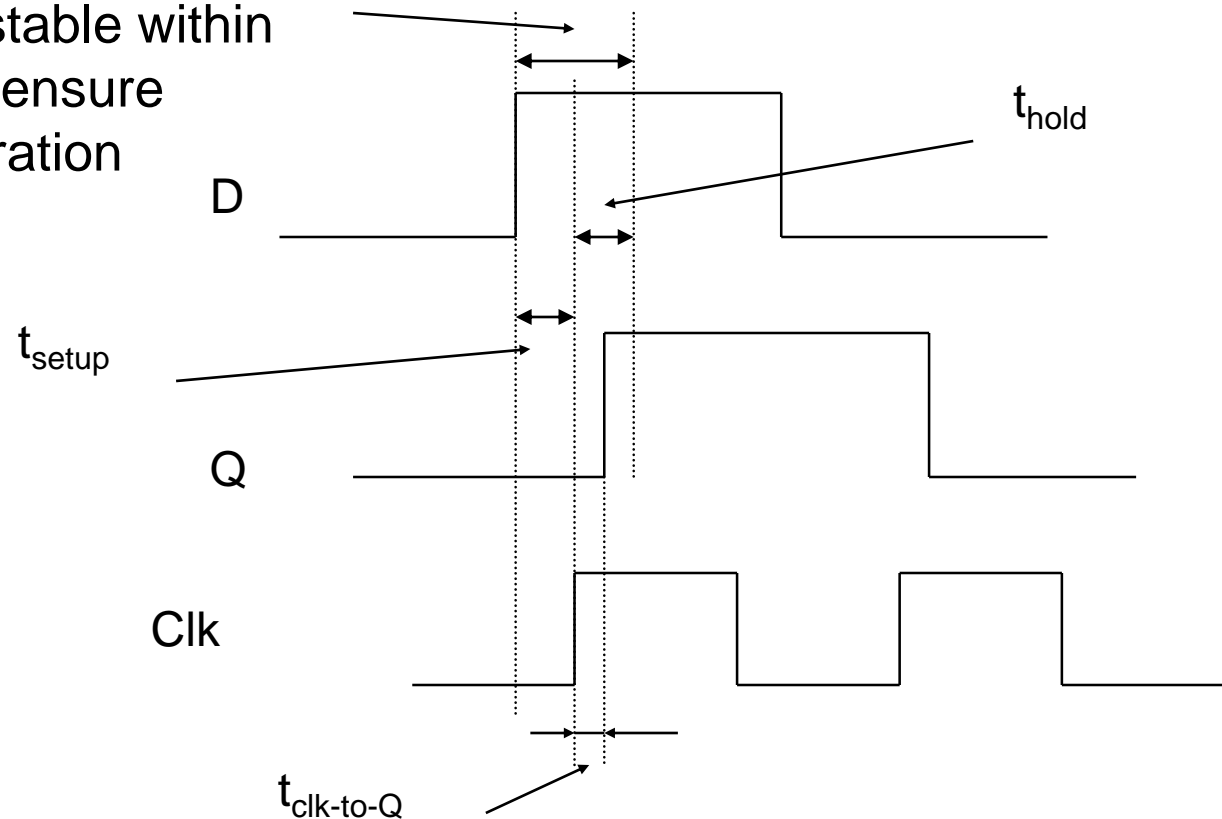D must be stable within this area to ensure correct operation



How do we create a sequence?


- We get a sequence if we take a value and then determine the next value based on the current value.

Ex: 0,1,0,1, ...

the next value = NOT (present value)

- We need to process (invert) the current value and then remember it until the next value is calculated


Sequential machines (cont.)

 

Problems !!! If CLK is 1 for a long time, values with a period of $T_{\text{latch}} + T_{\text{NOT}}$ just spin around

We want to design a storage element which changes its state no more than once during one clock cycle

Master-slave D-flip flop

 


Clk	D	Q(t+1)
↓	0	0
↓	1	1
1	x	Q(x)
0	x	Q(x)
↑	x	Q(x)



Inversion ring at CLK indicates a negative edge.

Negative edge triggered D-flip flop

 
Solution: Connect the two D-latches after each other!




Timing Chart Master-slave

  

Positive edge-triggered D flip-flop

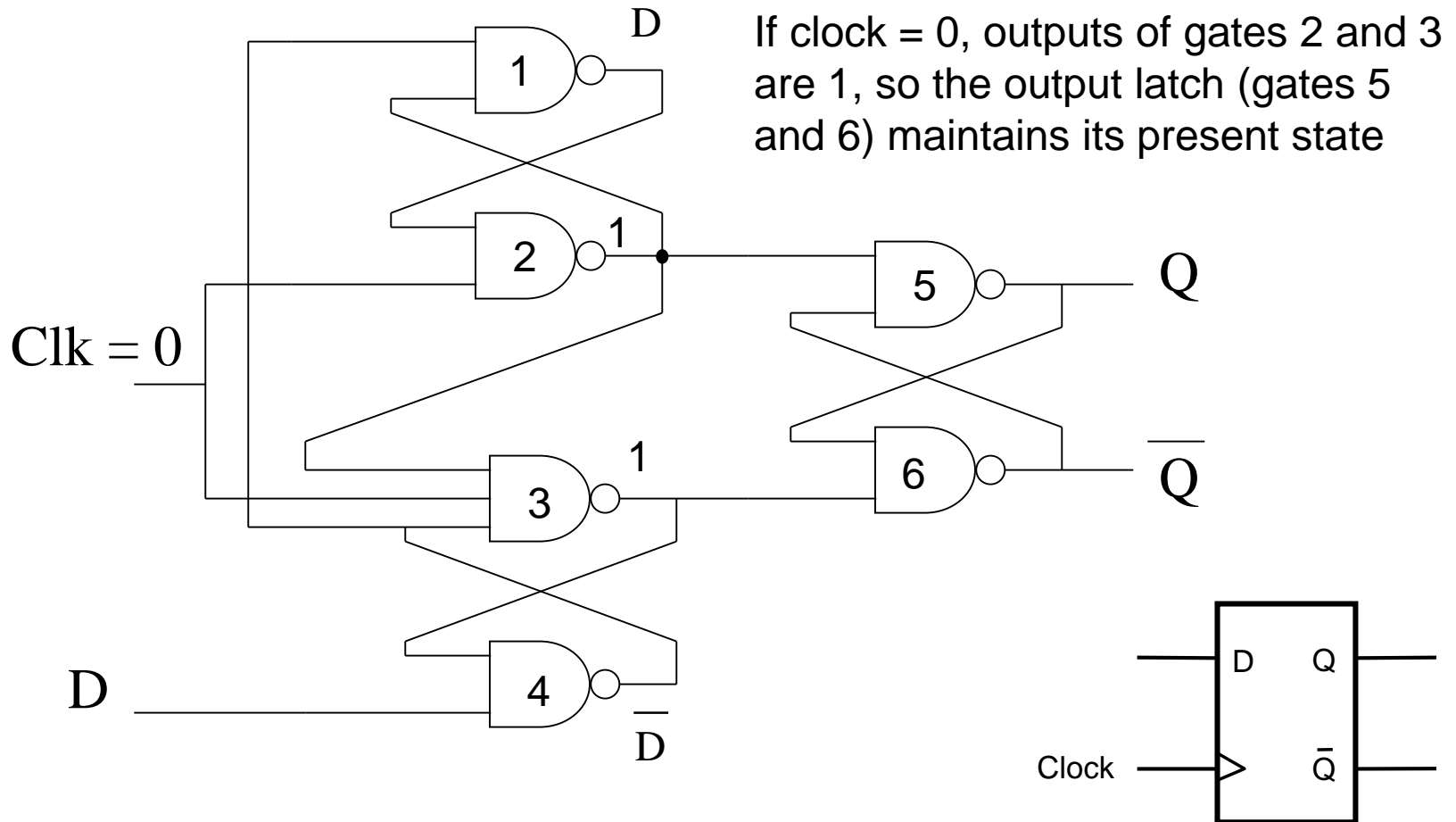


Positive edge-triggered D flip-flop

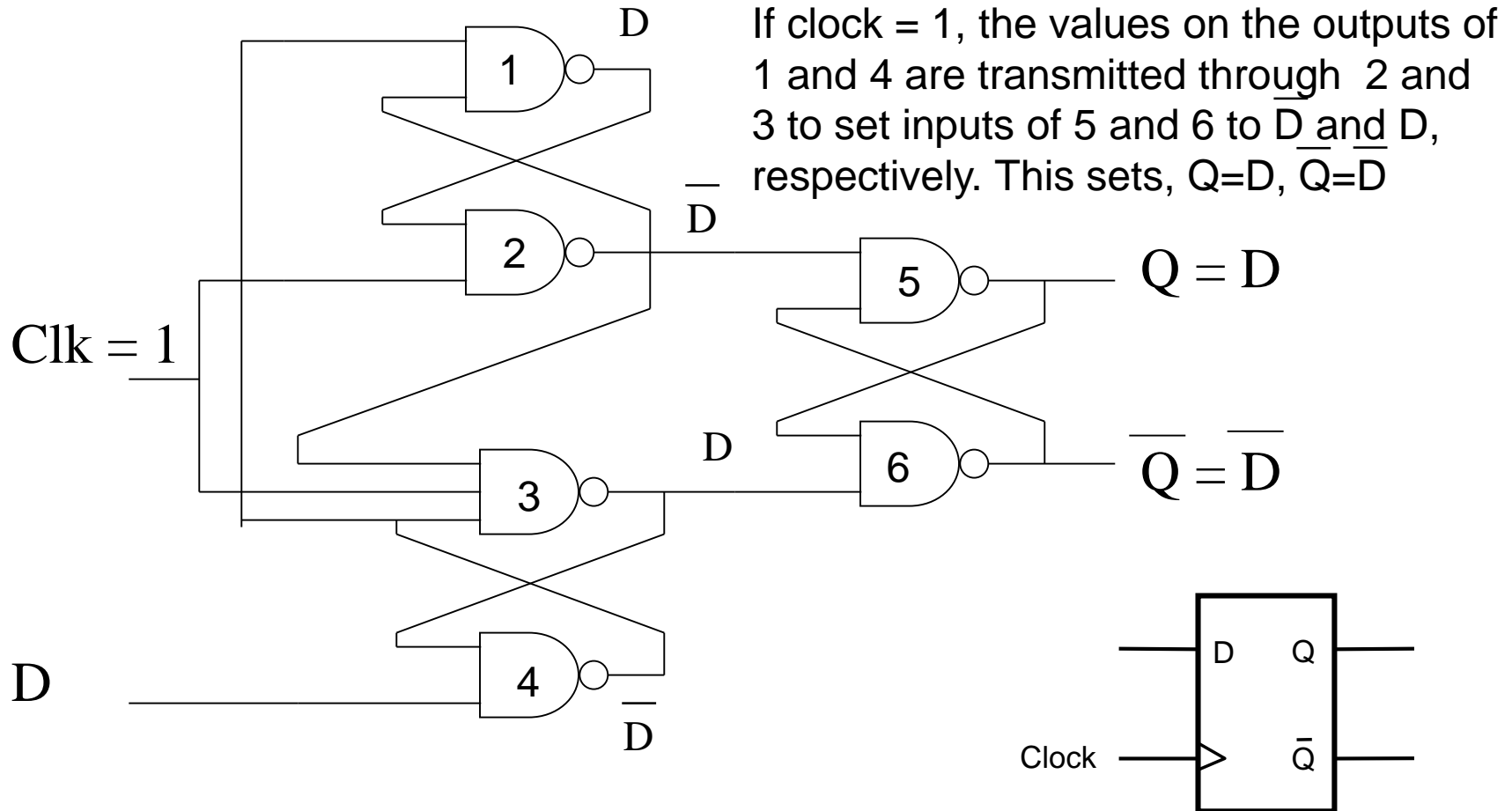



Flip-Flops with Clear and Preset inputs

 - It is important for the design sequential circuits to be able to set flip-flops to predetermined values
 - Preset: Sets the flip-flop to 1
 - Clear: Sets the flip-flop to 0




Asynchronous reset

  - An asynchronous reset (clear) means that the flip-flop will change its state to 0 immediately after the reset is active




Synchronous reset

 - A synchronous reset causes the flip-flop to take state 0 at the next clock edge
- Synchronous reset is implemented with an additional logic




Other common types of flip-flops

 JK flip-flop (by Jack Kilby - Nobel Prize 2000)



Clk	J	K	Q	\overline{Q}
↓	0	0	Q(t)	Q(t)
↓	0	1	0	1
↓	1	0	1	0
↓	1	1	$\overline{Q(t)}$	$\overline{Q(t)}$


T-flip-flop (T = Toggle)

 

Clk	T	Q	\overline{Q}
↓	0	Q(t)	Q(t)
↓	1	$\overline{Q(t)}$	$\overline{Q(t)}$


Construction of new flip-flops

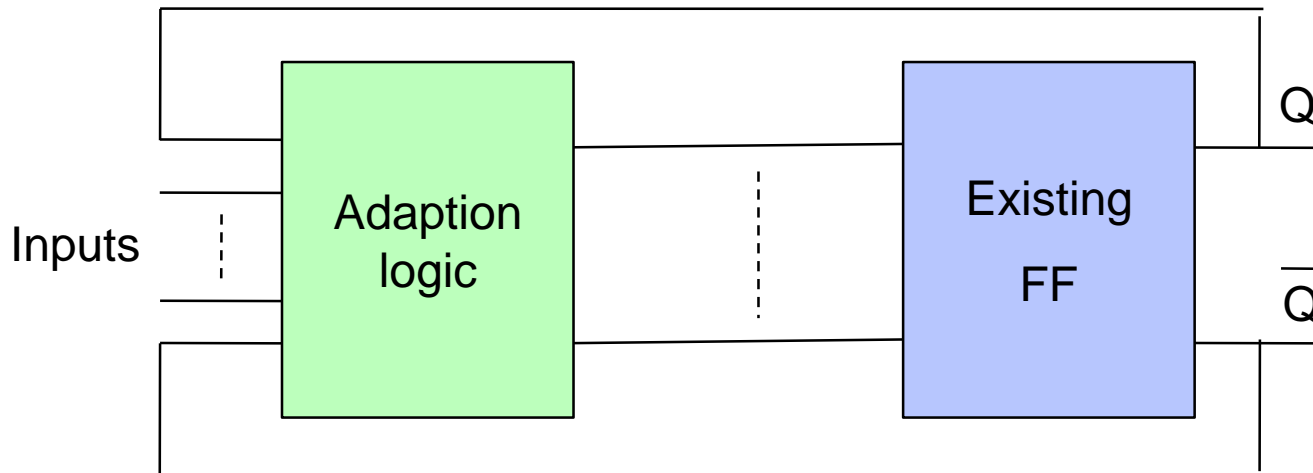- One can construct new flip-flops based on the existing types



Construction of the T flip-flop with D flip-flop

 - One can construct the new flip-flops based on an existing type



Clk	D	Q(t+1)
↑	0	0
↑	1	1

Clk	T	Q(t+1)
↑	0	$\overline{Q(t)}$
↑	1	$Q(t)$


Toggles at each positive edge of clock

Timing Analysis

- It is possible to determine the maximum frequency in a sequential circuit by having information about
 - Gate delays t_{logic}
 - Setup time t_{su} of flip-flops
 - Hold time t_{h} of flip-flops
 - Clock-to-output t_{cQ} time


Setup & Hold Time

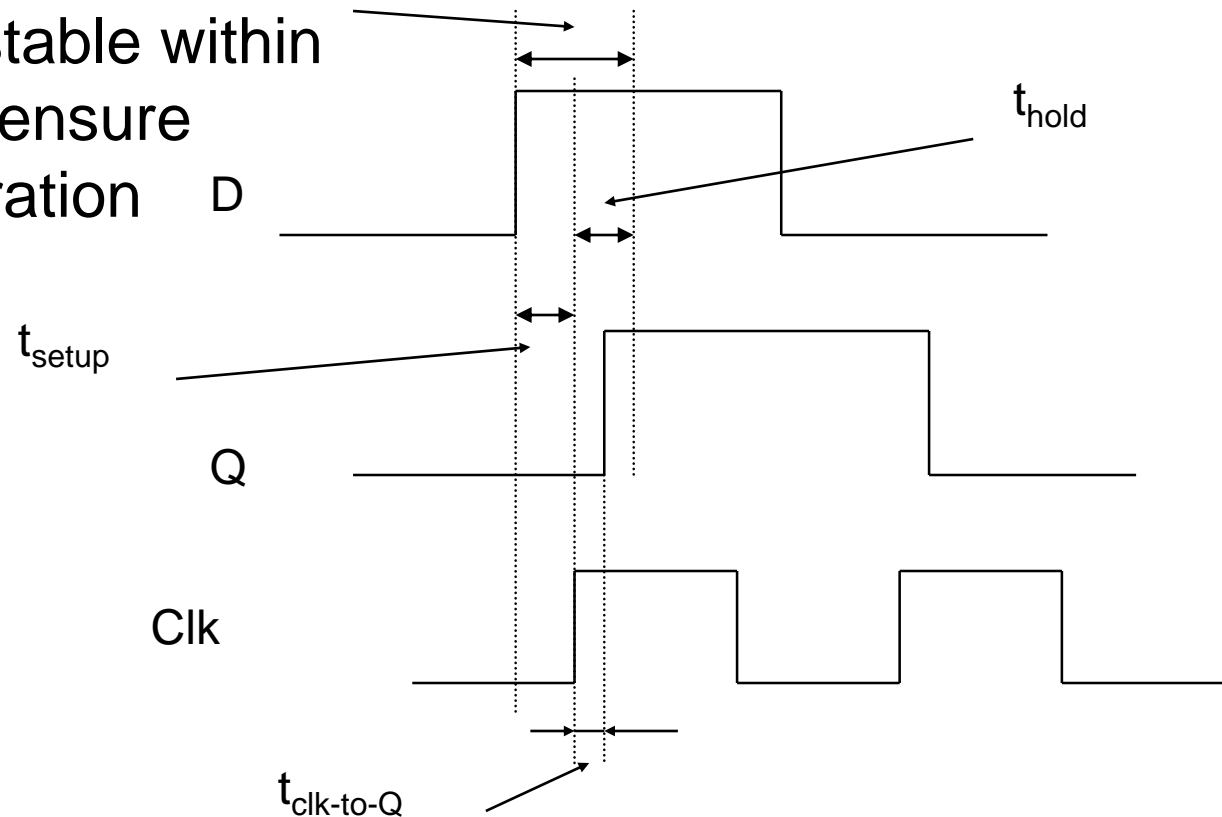D must be stable within
this area to ensure
correct operation



What is the maximum frequency?

 - Gate delays
 - $t_{\text{logic}} = t_{\text{NOT}} = 1.1 \text{ ns}$
- Setup time
 - $t_{\text{su}} = 0.6 \text{ ns}$
- Hold time
 - $t_{\text{h}} = 0.4 \text{ ns}$
- Clock-to-output
 - $t_{\text{cQ}} = 1.0 \text{ ns}$




$$T = t_{\text{su}} + \max(t_{\text{h}}, t_{\text{cQ}}) + t_{\text{logic}} = 2.7 \text{ ns}$$

$$F = 1/T = 370 \text{ MHz}$$


Shift Register

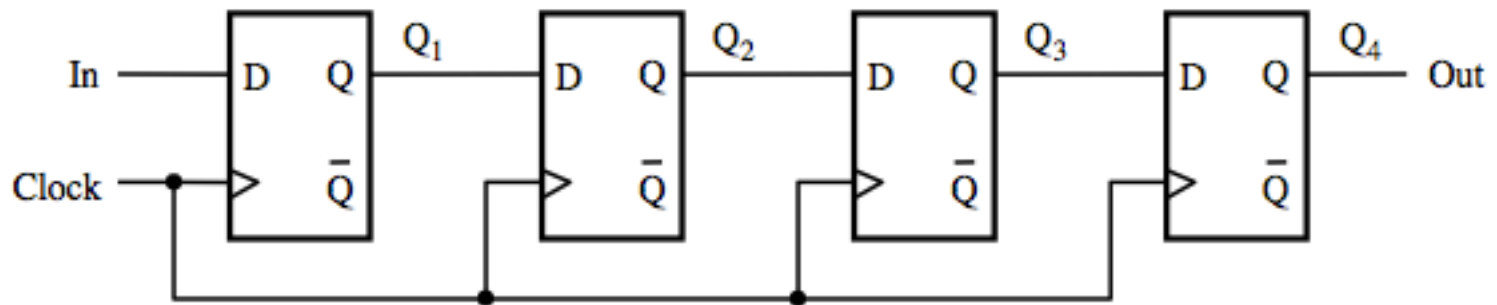- A shift register contains several flip-flops
- For each clock cycle, we shift all values from left to right
- Many designs use shift registers and values Q_4, \dots, Q_1 as input to other components



Asynchronous counter



- One can realize a counter with flip-flops
- The examples below show an *asynchronous* counter
- Some clock inputs are coupled to the \bar{Q} output of the previous flip-flop

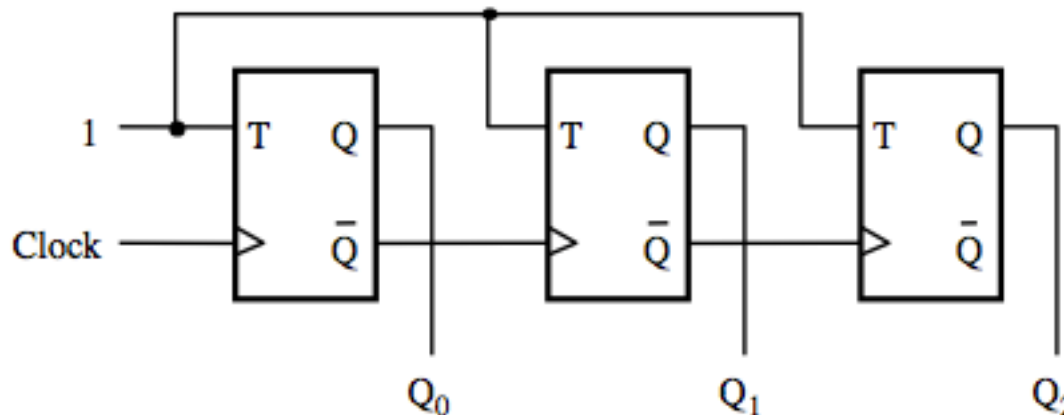

Asynchronous 3-bit counter


Clk	T	$Q(t+1)$
\uparrow	0	$\overline{Q(t)}$
\uparrow	1	$Q(t)$

Toggles at
each positive
edge of clock

 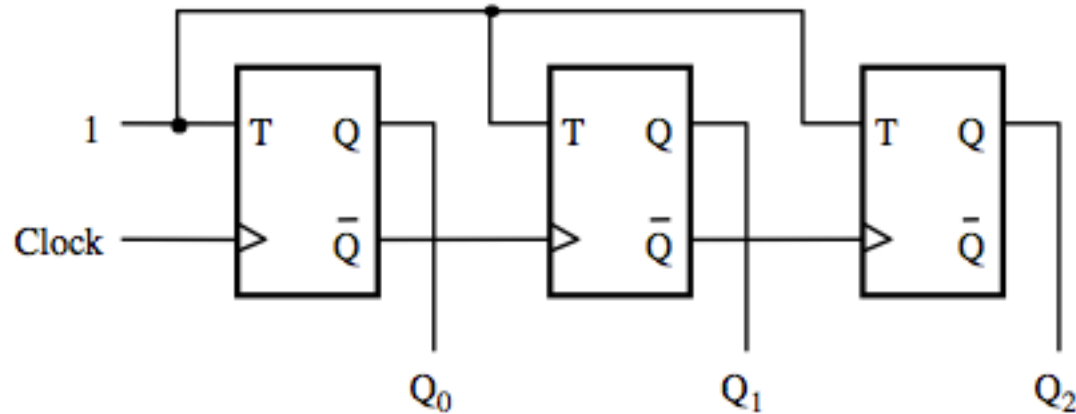

Synchronous counter


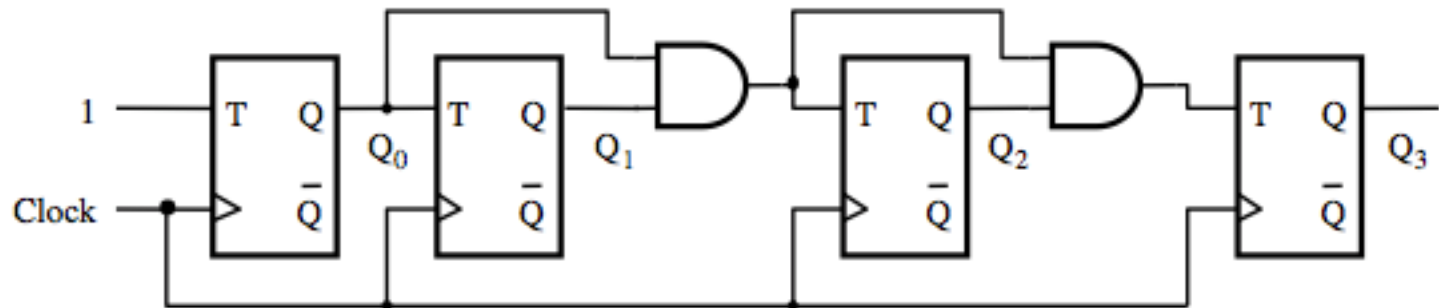
- In a *synchronous* counter clock inputs of flip-flops are connected to the same clock signal




Synchronous counter

Clk	T	$Q(t+1)$
↑	0	$Q(t)$
↑	1	$\overline{Q(t)}$

Toggles at
each positive
edge of clock

 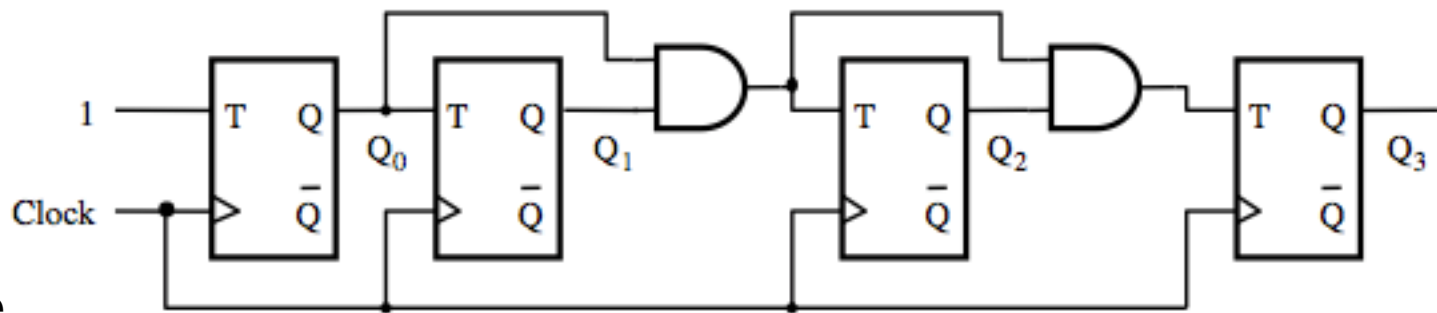

What is the maximum frequency?

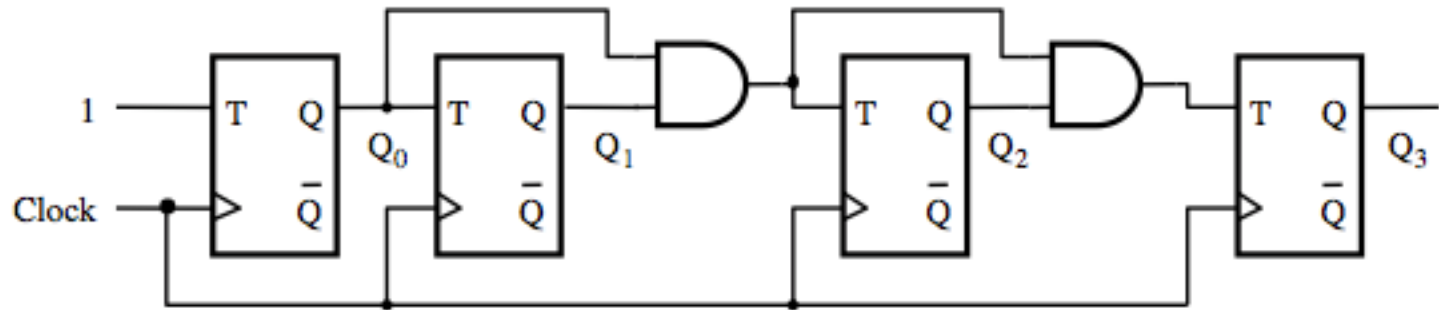

- The critical path determines the maximum frequency!
- This is the longest combinational path from Q_0 through the two AND gates to the input of flip-flop that computes Q_3
 - t_{logic} thus is equivalent to the delay of two AND gates

Summary

- Memory Elements
 - Latches
 - Flip-Flops
- Shift registers
- Counters
- Next lecture: BV pp. 485-507